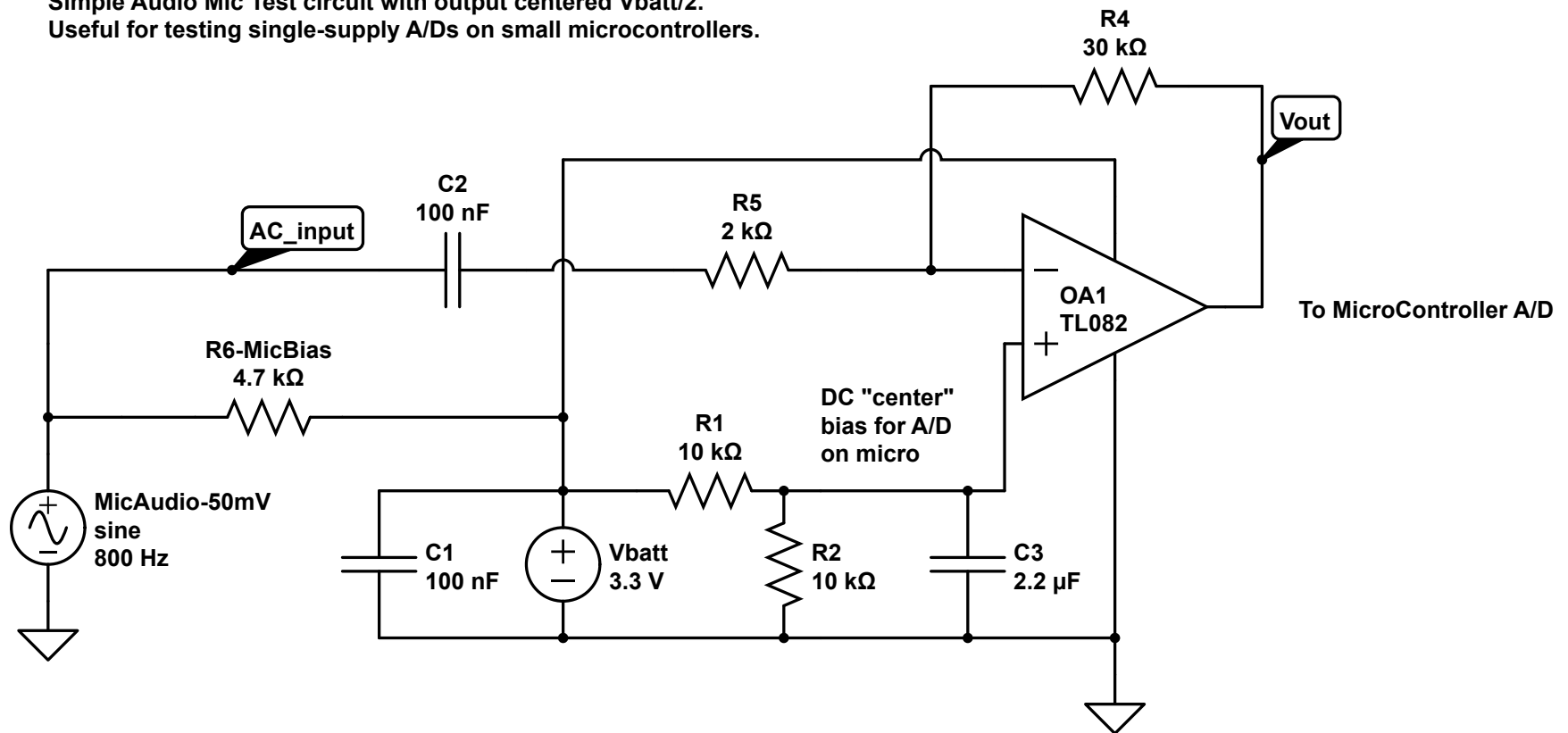


Simple Audio Mic Test circuit with output centered $V_{batt}/2$.
Useful for testing single-supply A/Ds on small microcontrollers.



M A Chatterjee 2012
This circuit is in the public domain.